

**Class : 9<sup>th</sup>**

**Subject : Computer Science**

**Chapter : 3     Digital Systems and Logic Design**

**Book Exercise Complete Solved**

**Punjab Board**

**1. Which of the following Boolean expressions represents the OR operation?**

✓ **Correct Answer: (b)  $A + B$**

**Options:**

(a)  $A \cdot B$

✓ (b)  $A + B$

(c)  $A$

(d)  $A \oplus B$

**Explanation:**

OR operation is represented by + sign in Boolean algebra  $\rightarrow A + B$ .

---

**2. What is the dual of the Boolean expression  $A \cdot 0 = 0$ ?**

✓ **Correct Answer: (a)  $A + 1 = 1$**

**Options:**

✓ (a)  $A + 1 = 1$

(b)  $A \cdot 1 = A$

(c)  $A + 1 = A$

(d)  $A \cdot 0 = 0$

**Explanation:**

In dual, replace  $\cdot$  with +, and 0 with 1:

$A \cdot 0 = 0 \rightarrow \text{Dual} = A + 1 = 1$

---

**3. Which logic gate outputs true only if both inputs are true?**

✓ **Correct Answer: (b) AND gate**



**Options:**

- (a) OR gate
- ✓ (b) AND gate
- (c) XOR gate
- (d) NOT gate

**Explanation:**

AND gate outputs 1 only when both inputs are 1.

---

**4. In a half-adder circuit, the carry is generated by which operation?**

✓ **Correct Answer: (b) AND operation**

**Options:**

- (a) XOR operation
- ✓ (b) AND operation
- (c) OR operation
- (d) NOT operation

**Explanation:**

Carry =  $A \cdot B \rightarrow$  AND operation

---

**5. What is the decimal equivalent of the binary number 1101?**

✓ **Correct Answer: (c) 13**

**Options:**

- (a) 11
- (b) 12
- ✓ (c) 13
- (d) 14

**Explanation:**

$1101_2 = (1 \times 8) + (1 \times 4) + (0 \times 2) + (1 \times 1) = 8 + 4 + 0 + 1 = 13$

## Short Questions

**1. Define a Boolean function and give an example.**

A Boolean function uses Boolean algebra and returns either 0 or 1.

**Example:**  $F = A + B$

**2. What is the significance of the truth table in digital logic?**

A truth table lists all possible inputs and their corresponding output, helping to understand and design logical circuits.



3. Explain the difference between analog and digital signals.

- **Analog signal:** Continuous and varies over time (e.g., sound waves).
- **Digital signal:** Discrete values (0 and 1), used in computers and electronics.

4. Describe the function of a NOT gate with its truth table.

The NOT gate inverts the input.

Input (A)	Output ( $\neg A$ )
0	1
1	0

5. What is the purpose of a Karnaugh map in simplifying Boolean expressions?

Karnaugh maps (K-maps) visually group terms in a Boolean expression to eliminate redundancy and simplify logic circuits.

## Long Question

1. Explain the usage of Boolean functions in computers.

**Answer:**

Boolean functions play a fundamental role in computers. They are used in:

- **Logic gates:** Every operation in a computer (AND, OR, NOT, etc.) is defined by Boolean functions.
- **Decision making:** Computers use Boolean expressions to make decisions (e.g., if-else).
- **Digital circuits:** Boolean functions are the building blocks of circuits like adders, multiplexers, and memory.
- **Arithmetic operations:** Adders and ALUs (Arithmetic Logic Units) use Boolean logic to perform calculations.

Example:

$A + B$  = Sum using OR gate

$A \cdot B$  = Carry using AND gate

**Q: Describe how to construct a truth table for a Boolean expression with an example.**

 **Answer:**

A **truth table** is a table that shows **all possible input combinations** of a Boolean expression and the **corresponding output** for each combination. It helps in analyzing and designing logic circuits.

---



### ◆ Steps to Construct a Truth Table

#### ✓ Step 1: Identify the number of variables

- Count how many input variables are in the Boolean expression.
- **Example:** If the expression is  $F = A \cdot B$ , there are **2 variables** (A and B).

#### ✓ Step 2: Calculate total combinations

- Use the formula:  $2^n$ , where  $n$  is the number of variables.
- For 2 variables:  $2^2 = 4$  combinations.

#### ✓ Step 3: List all input combinations

- Write down all the binary combinations of inputs from 00 to 11.

#### ✓ Step 4: Solve the Boolean expression for each row

- Apply the Boolean logic (AND, OR, NOT, etc.) to each combination.

---

### ◆ Example: Boolean Expression $\rightarrow F = A + B$

This expression uses the **OR operation** (+).

---

### ◆ Truth Table for $F = A + B$

A	B	A + B (F)
---	---	-----------

0	0	0
---	---	---

0	1	1
---	---	---

1	0	1
---	---	---

1	1	1
---	---	---

---

### ◆ Explanation of Each Row:

- **Row 1:**  $A = 0, B = 0 \rightarrow A + B = 0$
- **Row 2:**  $A = 0, B = 1 \rightarrow A + B = 1$
- **Row 3:**  $A = 1, B = 0 \rightarrow A + B = 1$
- **Row 4:**  $A = 1, B = 1 \rightarrow A + B = 1$



(OR gate gives output 1 if **any input is 1.**)

---

◆ Another Example (With NOT & AND):

Let's solve:  $F = A \cdot B + \neg A$

**A B  $\neg A$   $A \cdot B$   $F = A \cdot B + \neg A$**

0 0 1 0 1

0 1 1 0 1

1 0 0 0 0

1 1 0 1 1

---

✓ Conclusion:

Truth tables are **essential tools** in Boolean algebra and computer science.  
They help in:

- Verifying Boolean expressions
  - Designing and simplifying logic circuits
  - Understanding input/output behavior
- 

Agar aap is ka **Urdu tarjuma, PDF version**, ya aur koi expression ka truth table chahen tu zaroor batao bhai — mein ready hoon!

You said:

bhai again solve kro aur question ko smjo wo bol kya rha h 3 truth table bna do usy tum kya kar rhy ho

ChatGPT said:

Shukriya bhai! Aap bilkul theek keh rahe ho — question ko properly samajhna zaroori hai.

**Question yeh keh raha hai:**

"Describe how to construct a truth table for a Boolean expression **with an example.**"

Aur **aap chahte ho ke 3 different Boolean expressions ke truth tables banaye jayein** — taake concept poora clear ho jaye.



---

## ✓ Detailed Answer: How to Construct a Truth Table (with 3 Examples)

### 📖 What is a Truth Table?

A **truth table** shows **all possible combinations** of input variables and the **corresponding output** of a Boolean expression. It is used to check the logic of expressions and circuits.

---

### ◆ Step-by-Step Method:

1. **Identify variables** in the expression (like A, B, C).
  2. **Count combinations**: For  $n$  variables  $\rightarrow 2^n$  rows in the truth table.
  3. **List all binary combinations** of inputs.
  4. **Apply the Boolean expression** for each row and write the output.
- 

### ◆ Example 1: $F = A + B$

(OR Operation)

A B A + B (F)

0 0 0

0 1 1

1 0 1

1 1 1

✓ **Explanation:** OR gate gives 1 if **any one input is 1**.

---

### ◆ Example 2: $F = A \cdot B$

(AND Operation)



**A B A · B (F)**

0 0 0

0 1 0

1 0 0

1 1 1

✓ **Explanation:** AND gate gives 1 **only if both inputs are 1.**

---

### ◆ **Example 3: $F = A \cdot B + \neg A$**

**(AND + OR + NOT Combination)**

**A B  $\neg A$   $A \cdot B$   $F = A \cdot B + \neg A$**

0 0 1 0 1

0 1 1 0 1

1 0 0 0 0

1 1 0 1 1

✓ **Explanation:**

- Row 1:  $A=0 \rightarrow \neg A=1$ ,  $A \cdot B=0 \rightarrow F = 0 + 1 = 1$
  - Row 4:  $A=1$ ,  $B=1 \rightarrow A \cdot B=1$ ,  $\neg A=0 \rightarrow F = 1 + 0 = 1$
- 

### ✓ **Conclusion:**

To construct a truth table:

- Identify variables.
- List all possible binary inputs.
- Apply the Boolean logic.
- Record the result for each case.



Truth tables help in designing **accurate and error-free logic circuits**.

3. Describe the concept of duality in Boolean algebra and provide an example to illustrate it.

**Answer:**

The **duality principle** in Boolean algebra states that every Boolean expression remains valid if we:

- Replace AND ( $\cdot$ ) with OR ( $+$ )
- Replace OR ( $+$ ) with AND ( $\cdot$ )
- Replace 0 with 1 and 1 with 0

**Example:**

Original:  $A + 0 = A$   
Dual:  $A \cdot 1 = A$

Both are valid identities in Boolean algebra.

✓ **Q4: Compare and contrast half-adders and full-adders, including their truth tables, Boolean expressions, and circuit diagrams.**

**Answer:**

Feature	Half-Adder	Full-Adder
Inputs	2 (A, B)	3 (A, B, Carry-in)
Outputs	Sum, Carry	Sum, Carry-out
Carry Handling	Only current bits	Also handles previous carry
Boolean Expr.	Sum = $A \oplus B$ Carry = $A \cdot B$	Sum = $A \oplus B \oplus C_{in}$ Carry = $A \cdot B + B \cdot C_{in} + A \cdot C_{in}$

**Truth Table (Full-Adder):**

A	B	Cin	Sum	Carry
0	0	0	0	0
0	1	0	1	0
1	0	0	1	0
1	1	0	0	1
0	0	1	1	0
0	1	1	0	1
1	0	1	0	1




A	B	Cin	Sum	Carry
1	1	1	1	1

**Circuit diagrams** show Half-Adder using XOR & AND gates; Full-Adder using two Half-Adders and one OR gate.

#### ◆ Circuit Diagrams:

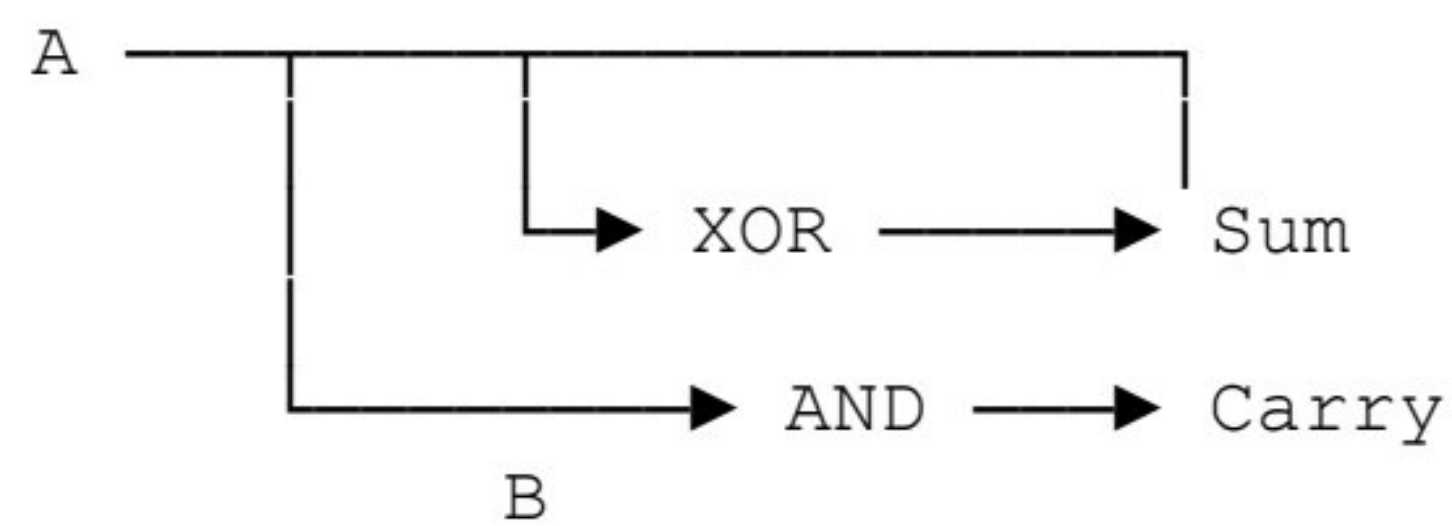
##### ◆ Half-Adder Circuit:

- One **XOR gate** for Sum
- One **AND gate** for Carry


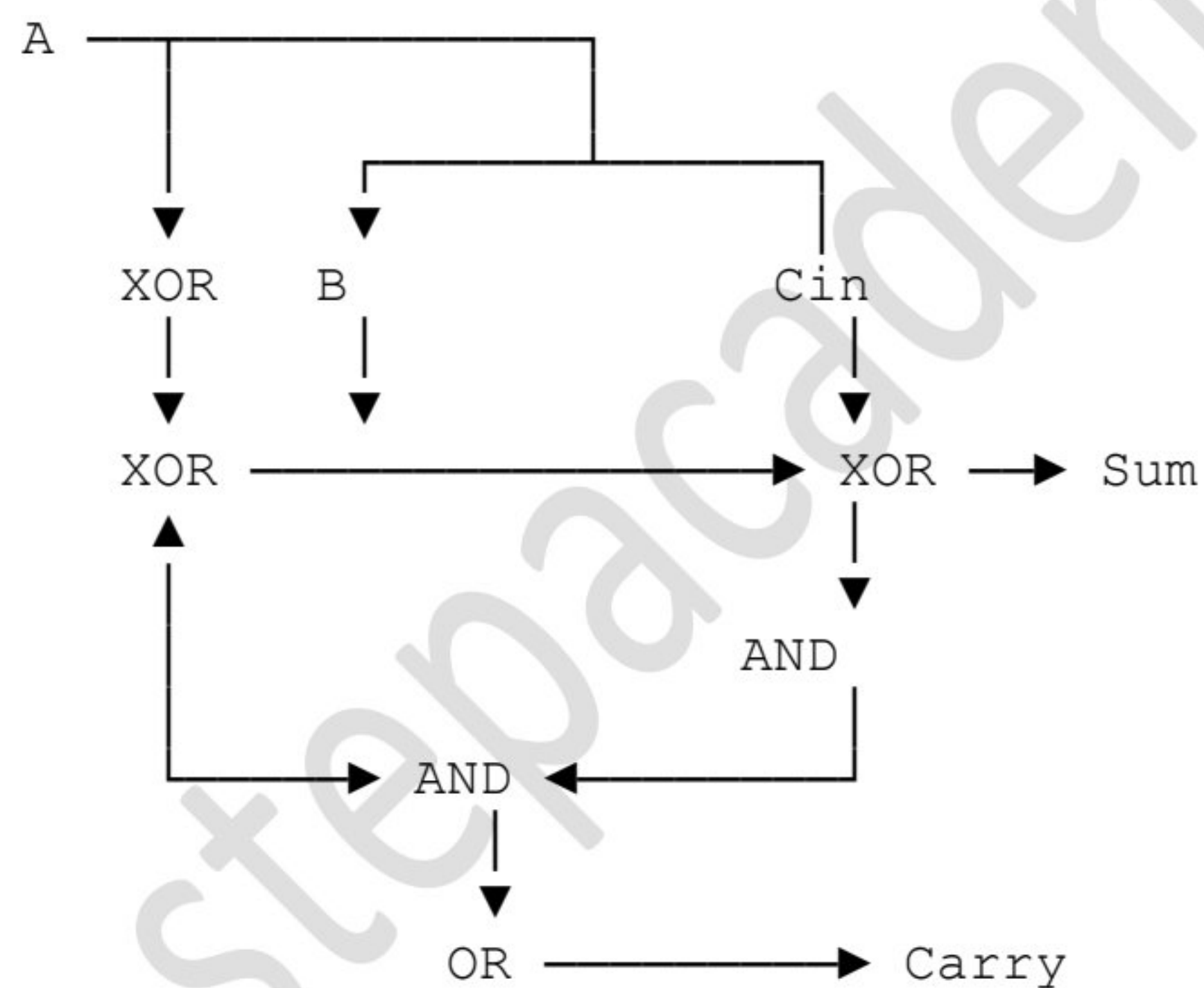
##### ◆ Full-Adder Circuit:

- Two **half-adders**
- One **OR gate** for final Carry



#### ✓ Conclusion:

- A **half-adder** adds only two bits and cannot process carry input.
- A **full-adder** handles carry input and is used in constructing multi-bit adders like **4-bit binary adders**.
- Both are essential components in **digital circuits and arithmetic units**.



5. How do Karnaugh maps simplify Boolean expressions? Provide a detailed example with steps.

**Answer:**

**Karnaugh Map (K-Map)** is a diagram used to simplify Boolean expressions.

Basic Rules:

1. Group only 1s (not 0s)
2. Groups must contain **1, 2, 4, or 8** boxes (powers of 2)
3. Groups should be **as large as possible**
4. Wrap-around grouping is allowed
5. Each 1 must be included at least once

### ◆ Example: Simplify $F(A, B) = \Sigma(1, 2, 3)$

This means the function  $F$  is 1 when the minterms (decimal values) **1, 2, and 3** are true.

◆ Step 1: Create the 2-variable K-Map

**AB 00 01 11 10**

**F 0 1 1 1**

Here:

- Cell 00  $\rightarrow F = 0$
- Cell 01  $\rightarrow F = 1$  (minterm 1)
- Cell 10  $\rightarrow F = 1$  (minterm 2)
- Cell 11  $\rightarrow F = 1$  (minterm 3)

◆ Step 2: Draw and Group the 1s

Group the 1s into **largest possible rectangle of 2 or 4**:

- Group 1: Cell 10 ( $A=1, B=0$ ) and Cell 11 ( $A=1, B=1$ )  $\rightarrow$  Common:  $A=1$
- Group 2: Cell 01 and 11  $\rightarrow$  Common:  $B=1$

◆ Step 3: Write the Simplified Expression

From groups:

- Group 1  $\rightarrow A$



- Group 2 → B

✓ **Simplified Expression:**  $F = A + B$

**6. Design a 4-bit binary adder using both half-adders and full-adders. Explain each step with truth tables, Boolean expressions, and circuit diagrams.**

A **4-bit binary adder** is a digital circuit that adds **two 4-bit binary numbers**. For example:

$$\begin{aligned} A &= A_3 \ A_2 \ A_1 \ A_0 \\ B &= B_3 \ B_2 \ B_1 \ B_0 \end{aligned}$$

It produces a **4-bit sum** ( $S_3 \ S_2 \ S_1 \ S_0$ ) and a **carry-out** from the last bit.

◆ **Components Used:**

- 1 **Half-Adder** for the first (least significant) bit
- 3 **Full-Adders** for the remaining bits

◆ **Structure:**

Bit Position	Adder Type	Inputs	Outputs
Bit 0 (LSB)	Half-Adder	A0, B0	S0, Carry0
Bit 1	Full-Adder	A1, B1, Carry0	S1, Carry1
Bit 2	Full-Adder	A2, B2, Carry1	S2, Carry2
Bit 3 (MSB)	Full-Adder	A3, B3, Carry2	S3, Carry3 (final carry)

◆ **Boolean Expressions:**

✓ *Half-Adder (Bit 0):*

- Sum ( $S_0$ ) =  $A_0 \oplus B_0$
- Carry0 =  $A_0 \cdot B_0$

✓ *Full-Adder (Bits 1 to 3):*

For each full-adder:

- Sum ( $S$ ) =  $A \oplus B \oplus C_{in}$



•  $Carry = (A \cdot B) + (C_{in} \cdot (A \oplus B))$

◆ Truth Table for Full-Adder (1-bit):

**A B C<sub>in</sub> Sum Carry**

0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

◆ Circuit Design:

✓ Half-Adder (Bit 0):

- XOR gate for Sum ( $A_0 \oplus B_0$ )
- AND gate for Carry ( $A_0 \cdot B_0$ )

✓ Full-Adders (Bits 1–3):

Each full-adder consists of:

- Two XOR gates
- Two AND gates
- One OR gate

Each bit receives:

- Two inputs (A and B)
- One carry from the previous bit

◆ Block Diagram Overview:

markdown

CopyEdit





B3	B2	B1	B0

Carry3   S3   S2   S1   S0

- **HA** = Half-Adder
- **FA** = Full-Adder
- The final output is a **5-bit result**: Carry3 + S3 S2 S1 S0

✓ Conclusion:

A 4-bit binary adder is constructed by:

- Using **1 Half-Adder** for the first bit
- Using **3 Full-Adders** for the next bits
- Connecting the **carry-out of each adder** to the **carry-in of the next**

This circuit is the basic building block of digital devices like **ALUs**, **calculators**, and **processors**.

7. Simplify the following Boolean function using Boolean algebra rules:

$$F(A, B) = A \cdot B + A \cdot B$$

**Answer:**

$$\begin{aligned} F &= A \cdot B + A \cdot B \\ &= A(B + B) \\ &= A \cdot 1 \end{aligned}$$

✓  $F = A$

8. Use De Morgan's laws to simplify the following function:

$$F(A, B, C) = \neg(A + B + AC)$$

**Answer:**

First, simplify inside:

$$A + B + AC = (A + B + A \cdot C)$$

Apply De Morgan's Law:

$$\neg(A + B + AC) = \neg A \cdot \neg B \cdot \neg(A \cdot C)$$



Now apply De Morgan's to last term:

$$\neg(A \cdot C) = \neg A + \neg C$$

So,

$$F = \neg A \cdot \neg B \cdot (\neg A + \neg C)$$

✓ Final simplified expression.

---

9. Simplify the following expressions:

(a)  $A + B \cdot (A + B)$

$$= A + A \cdot B + B \cdot B$$

$$= A + A \cdot B + B$$

$$= A + B \text{ (Using Absorption Law)}$$

✓  $A + B$

---

(b)  $(A + B) \cdot (A + B)$

$$= A + B \text{ (Idempotent Law)}$$

✓  $A + B$

---

(c)  $A + A \cdot (B + C)$

$$= A \text{ (Using Absorption Law)}$$

✓  $A$

---

(d)  $A \cdot B + A \cdot B$

$$= A \text{ (Using Rule: } A \cdot B + A \cdot B = A \text{)}$$

✓  $A$

---

(e)  $(A \cdot B) + (A \cdot B)$

$$= A \cdot B \text{ (Idempotent Law)}$$

✓  $A \cdot B$

---



stepacademyofficial.com